

ELEC-374 Digital Systems Engineering
Laboratory Project

Winter 2018

Designing a Simple RISC Computer: Phase 3

1. Objectives

The purpose of this project is to design, simulate, implement, and verify a simple RISC Computer (Mini SRC). So far, you have designed and functionally simulated the Datapath portion of the Mini SRC (except for *nop* and *halt* instructions that you will test in this phase). Phase 3 of this project consists of adding and testing the Control Unit in Mini SRC. You are to design the Control Unit in VHDL or Verilog. Testing will be done by Functional Simulation.

2. Preliminaries

2.1 Control Unit

A block diagram of the Control Unit for Mini SRC is shown in Figure 1. The Control Unit is at the heart of the processor. It accepts as input those signals that are needed to operate the processor and provides as output all the control signals necessary to execute the instructions. The outputs from the Control Unit are the control signals that we have been using in the previous phases to generate control sequences for the instructions of the Mini SRC.

 


Figure 1: Block diagram of the Control Unit

The Control Unit generates the control signals from four principal sources:

- (a) The op-code fields of the IR
- (b) Signals from the Datapath such as CON_FF, and the condition code registers (if any)
- (c) Control step information such as signals T0, T1, ...
- (d) External inputs such as Stop, Reset, Done (if memory is slow), and other signals such as interrupts (if any)

The external *Reset* input should get the Mini SRC to an initial state, where all registers including PC in the Datapath are set to 0, the *Run* indicator is set to 1, and the processor starts at Step T0. As the clock continues to run, instructions should be fetched and executed one after the other until a *halt* instruction is encountered, at which point the control stepping process should be halted and the *Run* indicator is set to 0. Note that, the external *Stop* input signal works the same way as the *halt* instruction.

During T0, T1, and T2, the control signals that are asserted to implement the “instruction fetch” sequence are independent of the bits in the Instruction Register. For instance, in Step T0, the control signals PCout, MARin, IncPC and Zin are set to 1. In Step T1, the control signals Zlowout, PCin, Read, and MDRin are set to 1. In Step T2, the control signals MDRout and IRin are set to 1. However, from Step T3 onward, until the current instruction is completed, the control signals that are asserted are a function of both Step Ti and the op-code bits in the IR register.

In the following, you will see two different methods to design your Control Unit. There is a trade-off between the two methods. Method 1 is clearly the easier method, but it may generate more hardware. Of course, you are free to come up with your own design style, if you wish.

Method 1: It is possible to write the VHDL/Verilog code without worrying about the combinational logic expressions for each control signal. Therefore, the code will come clean and the instructions will be executed in the most efficient manner. However, it may generate more hardware. The following sample VHDL and Verilog code are provided as a starting point for this method, which you may need to verify and revise for your Control Unit:

-- this is the VHDL sample code for Method 1 for the Control Unit

LIBRARY ieee;

USE ieee.std_logic_1164.all;

ENTITY control_unit **IS** -- here, you will define the inputs and outputs to your Control Unit

PORT (Clock, Reset, Stop, ..., CON_FF:	IN	STD_LOGIC;
IR:	IN	STD_LOGIC_VECTOR(31 DOWNTO 0);
Gra, Grb, Grc, Rin, ..., Rout:	OUT	STD_LOGIC;
Yin, Zin, PCout, IncPC, ..., MARin:	OUT	STD_LOGIC;
Read, Write, ..., Clear:	OUT	STD_LOGIC;
ADD, AND, ..., SHR:	OUT	STD_LOGIC);

END control_unit;

ARCHITECTURE Behavior **of** control_unit **IS**

TYPE State **IS** (Reset_state, fetch0, fetch1, fetch2, add3, add4, add5, ...);

SIGNAL Present_state: State;

BEGIN

PROCESS (Clock, Reset) -- finite state machine

BEGIN

IF (Reset = '1') **THEN** -- reset the processor

```

        Present_state <= Reset_state;
    ELSIF (rising_edge(Clock)) THEN      -- if clock rising-edge
        CASE Present_state IS
            WHEN Reset_state =>
                Present_state <= fetch0;
            WHEN fetch0 =>
                Present_state <= fetch1;
            WHEN fetch1 =>
                Present_state <= fetch2;
            WHEN add3 =>
                Present_state <= add4;
            WHEN add4 =>
                Present_state <= add5;
            ⋮
            WHEN fetch2 =>      -- instruction decoding based on the opcode to set the next state
                CASE IR(31 DOWNTO 27) IS
                    WHEN "00011" =>      -- this is the add instruction
                        Present_state <= add3;
                    ⋮
                    WHEN OTHERS =>
                END CASE;
            WHEN OTHERS =>
        END CASE;
    END IF;
END PROCESS;

PROCESS (Present_state)      -- do the job for each state
BEGIN
    CASE Present_state IS      -- assert the required signals in each state
        WHEN Reset_state =>
            Gra <= '0';          -- initialize the signals
            Grb <= '0';
            Grc <= '0';
            Yin <= '0';
            ⋮
        WHEN fetch0 =>
            PCout <= '1';      -- see if you need to de-assert these signals
            MARin <= '1';
            IncPC <= '1';
            Zin <= '1';
        WHEN add3 =>
            Grb <= '1';
            Rout <= '1';
            Yin <= '1';
            ⋮
        WHEN nop =>
        WHEN OTHERS =>
    END CASE;
END PROCESS;
END Behavior;
-----
// this is the Verilog sample code for Method 1 for the Control Unit

```

```

`timescale 1ns/10ps
module control_unit (
    output reg    Gra, Grb, Grc, Rin, ..., Rout,    // here, you will define the inputs and outputs to your Control Unit
                Yin, Zin, PCout, IncPC, ..., MARin,
                Read, Write, ..., Clear,
                ADD, AND, ..., SHR,

    input         [31:0] IR,
    input         Clock, Reset, Stop, ..., Con_FF);
parameter       Reset_state = 4'b0000, fetch0 = 4'b0001, fetch1 = 4'b0010, fetch2 = 4'b0011,
                add3 = 4'b0100, add4 = 4'b0101, add5 = 4'b0110, ...;
    reg          [3:0] Present_state = Reset_state;    // adjust the bit pattern based on the number of states

always @(posedge Clock, posedge Reset)    // finite state machine; if clock or reset rising-edge
begin
    if (Reset == 1'b1) Present_state = Reset_state;
    else case (Present_state)
        Reset_state      :    Present_state = fetch0;
        fetch0           :    Present_state = fetch1;
        fetch1           :    Present_state = fetch2;
        add3             :    Present_state = add4;
        add4             :    Present_state = add5;
        ...
        fetch2           :    begin
                                case (IR[31:27]) // inst. decoding based on the opcode to set the next state
                                    5'b00011      :    Present_state = add3; // this is the add instruction
                                    ...
                                endcase
                            end
    endcase
end

always @(Present_state)    // do the job for each state
begin
    case (Present_state)    // assert the required signals in each state
        Reset_state: begin
            Reset_state: begin
                Gra <= 0; Grb <= 0; Grc <= 0; Yin <= 0;    // initialize the signals
                ...
            end
        fetch0: begin
            PCout <= 1;    // see if you need to de-assert these signals
            MARin <= 1;
            IncPC <= 1;
            Zin <= 0;
        end
        add3: begin
            Grb <= 1; Rout <= 1;
            Yin <= 0;
        end
        ...
    endcase
end
endmodule

```

Method 2: In this approach, you will need to derive all control signal setting conditions for all instructions. For this, you must examine all of the control sequences of the machine. The logic for each control signal is generated by going through the control sequences looking for every occurrence of that control signal and writing the Boolean equation for the signal. For example, the Zlowout signal occurs at T1 in all instructions, at T5 in *and*, *or*, *add*, *sub*, *mul*, *div*, *shr*, *shra*, *shl*, *ror*, *rol*, *ld*, and *ldi* instructions, and in some T states for other instructions. Therefore,

$$\text{Zlowout} = \text{T1} + \text{T5} \cdot (\text{AND} + \text{OR} + \text{ADD} + \text{SUB} + \text{MUL} + \text{DIV} + \text{SHR} + \text{SHRA} + \text{SHL} + \text{ROR} + \text{ROL} + \dots) + \dots$$

The problem with this approach is that the logic for each control signal may change with the addition of new instructions, therefore this approach is provided here merely for the sake of completeness. You are advised to use Method 1, especially if you intend to extend the scope of the project by adding new instructions, etc.

The following sample VHDL and Verilog code are provided as a starting point for Method 2, which you may need to verify and revise for your Control Unit:

-- this is the VHDL sample code for Method 2 for the Control Unit

LIBRARY ieee;

USE ieee.std_logic_1164.all;

ENTITY control_unit **IS** -- Here, you will define the inputs and outputs to your Control Unit

PORT (Clock, Reset, Stop, ..., CON_FF:	IN	STD_LOGIC;
IR:	IN	STD_LOGIC_VECTOR(31 DOWNTO 0);
Gra, Grb, Grc, Rin, ..., Rout:	OUT	STD_LOGIC;
Yin, Zin, PCout, IncPC, Zlowout, ..., MARin:	OUT	STD_LOGIC;
Read, Write, ..., Clear:	OUT	STD_LOGIC;
ADD, AND, ..., SHR:	OUT	STD_LOGIC);

END control_unit;

ARCHITECTURE Behavior **of** control_unit **IS**

SIGNAL T0, T1, T2, T3, T4, T5, ..., : STD_LOGIC;

SIGNAL ADD_s, SUB_s, AND_s, OR_s, ..., : STD_LOGIC;

TYPE State **IS** (Reset_state, S0, S1, ...,);

SIGNAL Present_state: State;

BEGIN

PROCESS (Clock, Reset, ...) -- finite state machine

BEGIN

IF (Reset = '1') **THEN** -- reset the processor

Present_state <= Reset_state;

ELSIF (rising_edge(Clock)) **THEN** -- if clock rising-edge

T0 <= '0'; T1 <= '0'; T2 <= '0'; T3 <= '0'; T4 <= '0'; T5 <= '0'; ...

CASE Present_state **IS**

WHEN Reset_state =>

Present_state <= S0;

T0 <= '1';

WHEN S0 =>

Present_state <= S1;

T1 <= '1';

⋮

```

        WHEN OTHERS =>
            END CASE;
        END IF;
    END PROCESS;

    PROCESS (IR)
    BEGIN
        ADD_s <= '0'; AND_s <= '0'; ...
        CASE IR(31 DOWNT0 27) IS -- inst. decoding based on the opcode
            WHEN "00011" =>
                ADD_s <= '1'; -- this is the add instruction
            WHEN "00101" =>
                AND_s <= '1'; -- this is the and instruction
            :
            WHEN OTHERS =>
                ;
        END CASE;
    END PROCESS;

    PROCESS (Clock, T0, T1, ...)
    BEGIN
        ADD <= ADD_s AND T4; -- control signal assignment
        Zlowout <= T1 OR (T5 AND (AND_s OR OR_s OR ADD_s OR SUB_s OR ...)) OR ...;
        :
    END PROCESS;
END Behavior;
-----

```

// this is the Verilog sample code for Method 2 for the Control Unit

```

`timescale 1ns/10ps
module control_unit (
    output reg    Gra, Grb, Grc, Rin, ..., Rout,    // here, you will define the inputs and outputs to your Control Unit
    Yin, Zin, PCout, IncPC, Zlowout, ..., MARin,
    Read, Write, ..., Clear,
    ADD, AND, ..., SHR,
    input         [31:0] IR,
    input         Clock, Reset, Stop, ..., Con_FF);

parameter       Reset_state = 4'b0000, S0 = 4'b0001, S1 = 4'b0010, ...;
reg             [3:0] Present_state = Reset_state;    // adjust the bit pattern based on the number of states
reg             T0, T1, T2, T3, T4, T5, ..., ;
reg             ADD_s, SUB_s, AND_s, OR_s, ..., :

always @(posedge Clock, posedge Reset, ...)    // finite state machine; if clock or reset rising-edge
begin
    if (Reset == 1'b1) Present_state = Reset_state;    // reset the processor
    else begin
        T0 <= 0; T1 <= 0; T2 <= 0; T3 <= 0; T4 <= 0; T5 <= 0;
        case (Present_state)
            Reset_state: begin
                Present_state = S0;
            end
        endcase
    end
end

```

```

        T0 <= 1;
    end
    S0: begin
        Present_state = S1;
        T1 <= 1;
    end
    ...
endcase
end
end

always @(IR)
begin
    ADD_s <= 0; AND_s <= 0; ...
    case (IR[31:27])
        5'b00011: ADD_s <= 1; // inst. decoding based on the opcode
        5'b00101: AND_s <= 1; // this is the add instruction
        // this is the and instruction
        ...
    endcase
end

always @(Clock, T0, T1, ...)
begin
    ADD <= ADD_s && T4; // control signal assignment
    Zlowout <= T1 || (T5 && (AND_s || OR_s || ADD_s || SUB_s || ...)) || ...;
    ...
end
endmodule

```

3. Procedure

- 3.1)** Use one of the above Methods (or come up with your own design style) and write your VHDL/Verilog code to implement the Control Unit. Add the Control Unit to your Datapath.
- 3.2)** Run a functional simulation of the following program on Mini SRC and demonstrate it to one of the TAs. Note that this program is provided just for the sake of testing the control unit and the instructions in Mini SRC, except for brnz/brzr Branch and Input/Output instructions that will be included in the test code for Phase 4.

Encode your program in the memory with the starting address zero. Initialize the memory locations \$68 and \$52 with the 32-bit values \$55 and \$26, respectively.

Minimum outputs are IR, PC, MDR, MAR, R0 – R15, HI, and LO. Add any other signals you would like to observe to convince yourself that your design works perfectly.

```

ORG    0
ldi    R1, 2        ; R1 = 2
ldi    R0, 0(R1)    ; R0 = 2
ld     R2, $68      ; R2 = ($68) = $55

```

	ldi	R2, -4(R2)	; R2 = \$51
	ld	R1, 1(R2)	; R1 = (\$52) = \$26
	ldi	R3, \$69	; R3 = \$69
	brmi	R3, 4	; continue with the next instruction (will not branch)
	ldi	R3, 2(R3)	; R3 = \$6B
	ld	R7, -3(R3)	; R7 = (\$6B - 3) = \$55
	nop		
	brpl	R7, 2	; continue with the instruction at "target" (will branch)
	ldi	R2, 5(R0)	; this instruction will not execute
	ldi	R3, 2(R1)	; this instruction will not execute
target:	add	R3, R2, R3	; R3 = \$BC
	addi	R7, R7, 2	; R7 = \$57
	neg	R7, R7	; R7 = \$FFFFFFA9
	not	R7, R7	; R7 = \$56
	andi	R7, R7, \$0F	; R7 = 6
	ror	R1, R1, R0	; R1 = \$80000009
	ori	R7, R1, \$1C	; R7 = \$8000001D
	shra	R7, R7, R0	; R7 = \$E0000007
	shr	R2, R3, R0	; R2 = \$2F
	st	\$52, R2	; (\$52) = \$2F new value in memory with address \$52
	rol	R2, R2, R0	; R2 = \$BC
	or	R2, R3, R0	; R2 = \$BE
	and	R1, R2, R1	; R1 = \$8
	st	\$60(R1), R3	; (\$68) = \$BC new value in memory with address \$68
	sub	R3, R2, R3	; R3 = 2
	shl	R1, R2, R0	; R1 = \$2F8
	ldi	R4, 6	; R4 = 6
	ldi	R5, \$32	; R5 = \$32
	mul	R5, R4	; HI = 0; LO = \$12C
	mfhi	R7	; R7 = 0
	mflo	R6	; R6 = \$12C
	div	R5, R4	; HI = 2, LO = 8
	ldi	R8, -1(R4)	; R8 = 5 setting up argument registers
	ldi	R9, -19(R5)	; R9 = \$1F R8, R9, R10, and R11
	ldi	R10, 0(R6)	; R10 = \$12C
	ldi	R11, 0(R7)	; R11 = 0
	jal	R10	; address of subroutine subA in R10 - return address in R15
	halt		; upon return, the program halts
subA:	ORG	\$12C	; procedure subA
	add	R13, R8, R10	; R12 and R13 are return value registers – not used
	sub	R12, R9, R11	; R13 = \$131, R12 = \$1F
	sub	R13, R13, R12	; R13 = \$112
	jr	R15	; return from procedure

4. Report

The phase 3 report (one per group) consists of:

- Printouts of your Schematic (if any)
- Printouts of your VHDL or Verilog code
- Functional simulation run of the program
- Printouts of the contents of memory before and after the program run